

# DLD Online 1

Section B2

There are 6 boolean functions in the following page. **There are students ids written beside each problem.**

- You have to implement the boolean functions using **ONLY** the following IC chips in your circuit: ***IC 74x04, IC 74x08 and IC 74x32.***
- Each student will have to implement **only** the function having his/her student id written beside (Check next page).
- The online carries 10 Marks.
- Name your submission as STUDENT\_ID.circ (e.g., **1905006.circ**). Submit the file in the moodle.
- **Time: 30 minutes + 5 Minutes to submit in Moodle.** Submissions made after this period will not be evaluated.

**Step 1 (7):** Given a 4-bit Boolean input  $X=X_3X_2X_1X_0$ . Implement a Boolean function:  
 $F(X) =$

1.  $X_1'(X_3X_2+X_2'X_0)+X_3'X_0(X_2'+X_1)$  [student id: **91,97,103,109,115**]
2.  $X_1(X_3X_2+X_3'X_0)+X_3'X_2'(X_1'+X_0)$  [student id: **92,98,104,110,116**]
3.  $X_2(X_3'X_0+X_1X_0')+X_1X_0(X_3'+X_2')$  [student id: **93,99,105,111,117**]
4.  $X_2'(X_3X_1'+X_1X_0)+X_3'X_1(X_2+X_0)$  [student id: **94,100,106,112,118**]
5.  $X_3'(X_2'X_1'+X_2X_0)+X_2X_0(X_3+X_1')$  [student id: **95,101,107,113,119**]
6.  $X_3(X_2X_0'+X_1X_0)+X_1'X_0'(X_3'+X_2)$  [student id: **96,102,108,114,120**]

**Step 2 (1):** Create a circuit with 4 input bits  $X_3, X_2, X_1, X_0$  and 2 output bits  $F(X), F(X)'$ .  
(Hence, 4 input pins and 2 output pins)

**Step 3 (2):** For given two 4-bit Boolean inputs **A** and **B**, use the created circuit to calculate  $F(A)'F(B)+F(A)F(B)'$ . (2 input pins, each with 4 data bits)

# Evaluation

Problem	Teacher's Initial	Link
1 and 2	MB	<a href="https://bdren.zoom.us/j/64234432263">https://bdren.zoom.us/j/64234432263</a>
3 and 4	SSA	<a href="https://bdren.zoom.us/j/62038199284">https://bdren.zoom.us/j/62038199284</a>
5 and 6	MMM	<a href="https://bdren.zoom.us/j/64434053593?pwd=OXkrckUwNjdLUnBzU3VWOVUrTFpmdz09">https://bdren.zoom.us/j/64434053593?pwd=OXkrckUwNjdLUnBzU3VWOVUrTFpmdz09</a>